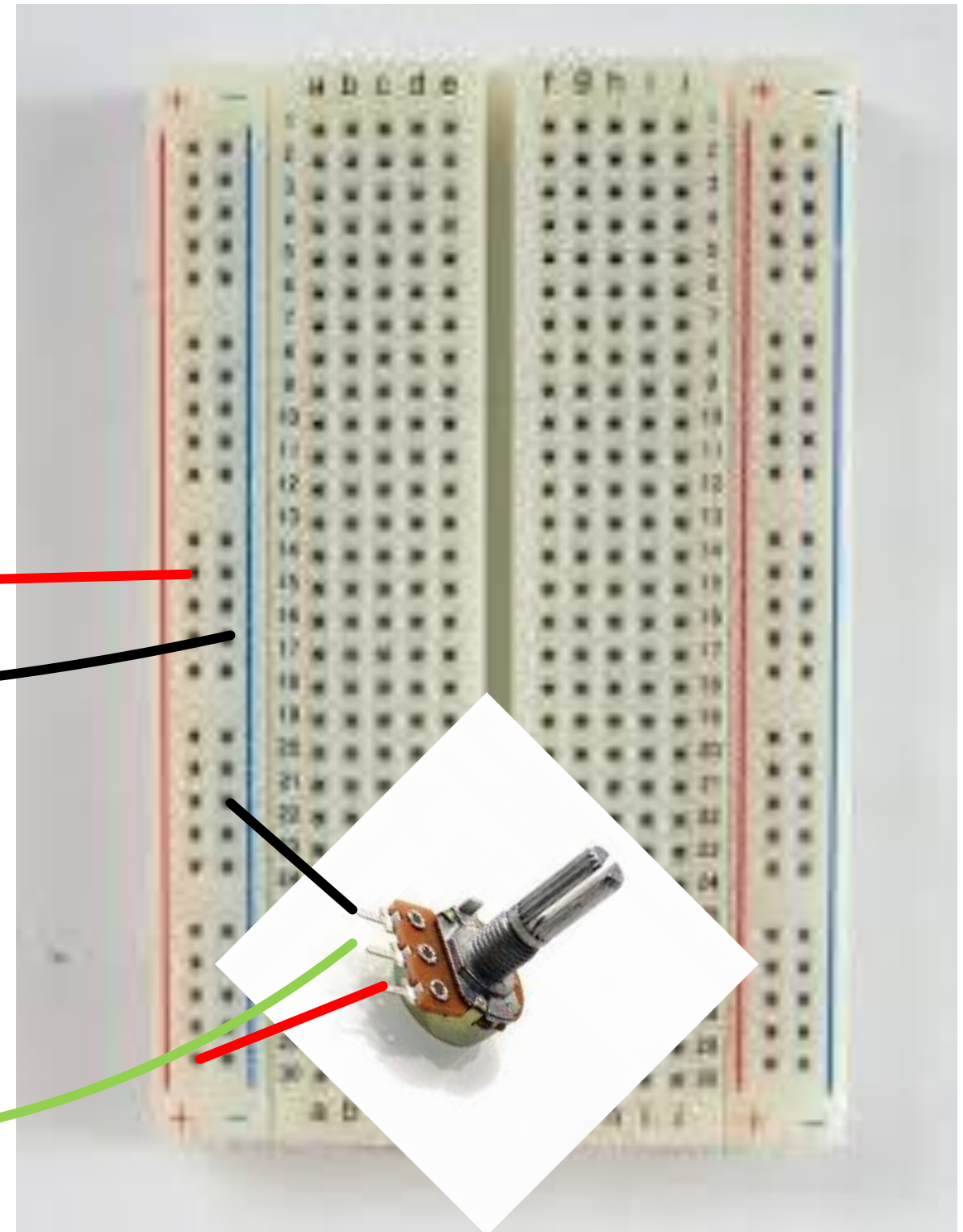


The 5-VDC is connected to the + strip on the breadboard (red)

The ground is connected to the – bus on the breadboard (blue)

A0, A1, A2 are connected to pin 3 on the breadboard



The potentiometer has 3 pins, 1 left, 2 centre, 3 right